



EE-224: Digital Design

IITB-CPU

Instructor: Prof. Virendra Singh

Team ID - 7

Aman Rishal CH – 22b3914

Aman Milind Moon – 22b1216

Chinmay Tripurwar – 22b3902

Swarup Dasharath Patil – 22b3953

Introduction

The IITB-CPU, crafted as a 16-bit computer system, is a foundational architecture designed for educational purposes, particularly for teaching Little Computer Architecture. Featuring eight general-purpose registers (R0 to R7), with Register R7 exclusively assigned to storing the Program Counter (PC), this compact CPU employs a memory addressing scheme where each address corresponds to a single byte. The architecture supports three distinct instruction formats: R, I, and J types, each tailored for specific tasks in executing machine code. In total, the IITB-CPU accommodates 14 instructions, making it a versatile and practical platform for educational exploration.

Major Components Used

1. **Memory**
The memory is organized as an array with 512 bytes, and each memory location holds 8 bits of data.
2. **Register File**
The register file consists of eight 16-bit registers of which register R7 is used as a program counter.
3. **5 Temporary registers**
The system employs four 16-bit temporary registers and one 3-bit register for quick and versatile data storage during computational tasks.
4. **Instruction Register**
The Instruction Register, a 16-bit storage unit, holds instructions in the r, i, or j format
5. **ALU**
The ALU (Arithmetic Logic Unit) performs operations like addition, subtraction, multiplication, logical OR, logical AND, and implication on two 16-bit numbers within the computer system.
6. **Sign Extender**
The sign extender extends either a 6-bit or 9-bit number to a 16-bit number based on the control signal, preserving the sign bit for accurate representation in the computer system.
7. **Shifter**
The shifter performs either left shifts or right shifts on binary data, governed by the control signal, within the computer system.

States

Description:

State 1: Read from memory and increment PC

State 2: Read Instruction (R Type)

State 3: Execute Specific ALU operation

State 4: Update Result

State 5: Read Instruction (LHI/LLI)

State 6: Read Instruction (ADI)

State 7: Read Instruction (LW/SW)

State 8: Read from memory

State 9: Write to memory

State 10: Branch to PC + Imm*2

State 11: PC to Reg. A


State 12: Branch to Reg. B

State Flowcharts

States	Data Transfer	Control Signal
S1	111 → RF_A1 RF_D1 → MEM_ADD MEM_OUT → IR RF_D1 → ALU_A +2 → ALU_B ALU_C → RF_D3 111 → RF_A3 RF_D1 → T5	M_RD IR_W ALU_CTRL RF_WR T5_WR
S2	IR_11_9 → RF_A1 IR_8_6 → RF_A2 RF_D1 → T1 RF_D2 → T2 IR_5_3 → T4	T1_WR T2_WR T4_WR
S3	T1 → ALU_A	ALU_CTRL


	T2 → ALU_B ALU_C → T3 ALU_Z → Zin	T3_WR
S4	T3 → RF_D3 T4 → RF_A3	RF_WR
S5	IR_8_0 → SHIFTER_IN SHIFTER_OUT → T3 IR_11_9 → T4	SHIFT_SIGNAL T3_WR T4_WR
S6	IR_11_9 → RF_A1 RF_D1 → T1 IR_8_6 → T4 IR_5_0 → SE_IN_6 SE_OUT → T2	T1_WR T2_WR SE_SIGNAL T4_WR
S7	IR_11_9 → T4 IR_5_0 → SE_IN_6 SE_OUT → ALU_A IR_8_6 → RF_A2 RF_D2 → ALU_B ALU_C → T3 IR_11_9 → RF_A1 RF_D1 → T1	T4_WR SE_SIGNAL ALU_CTRL T3_WR T1_WR
S8	T3 → MEM_ADD MEM_OUT → T3	M_RD
S9	T1 → MEM_IN T3 → MEM_ADD	M_WR
S10	T5 → ALU_A IR_5_0 → SE_IN_6 IR_8_0 → SE_IN_9 SE_OUT → SHIFTER_IN SHIFTER_OUT → ALU_B ALU_C → RF_D3 111 → RF_A3	SE_SIGNAL SHIFTER_SIGNAL ALU_CTRL RF_WR
S11	TR_11_9 → RF_A3 T5 → RF_D3	RF_WR
S12	IR_8_6 → RF_A2 RF_D2 → RF_D3 111 → RF_A3	RF_WR

FSM

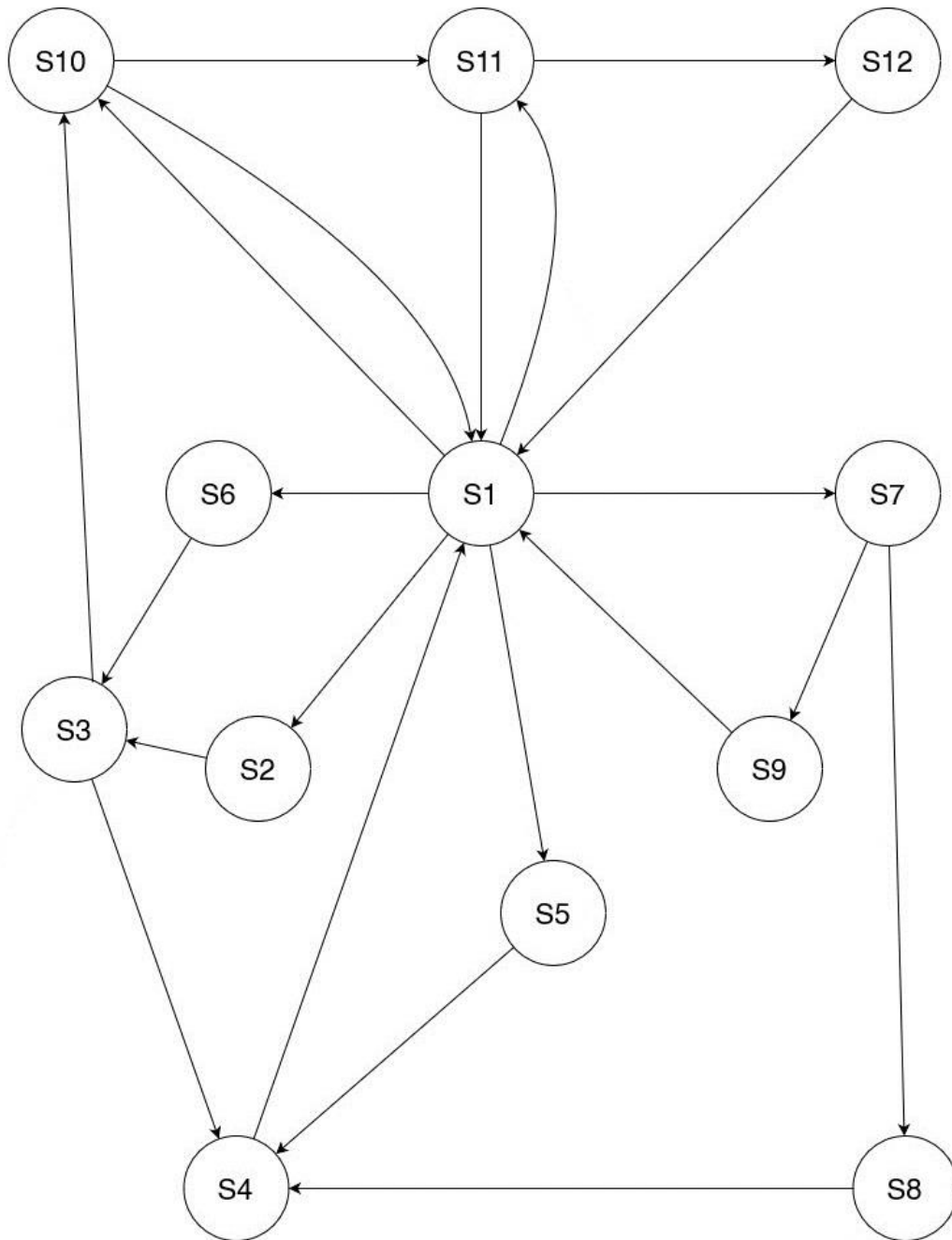


STATE FLOW DIAGRAM


ALU

 


J-Type

 

ADI

 


LW

 


Text is not SVG - cannot


SW

 


BEQ

 

JAL

 


JLR

 


RTL SIMULATIONS


ADD R1 R2 R3

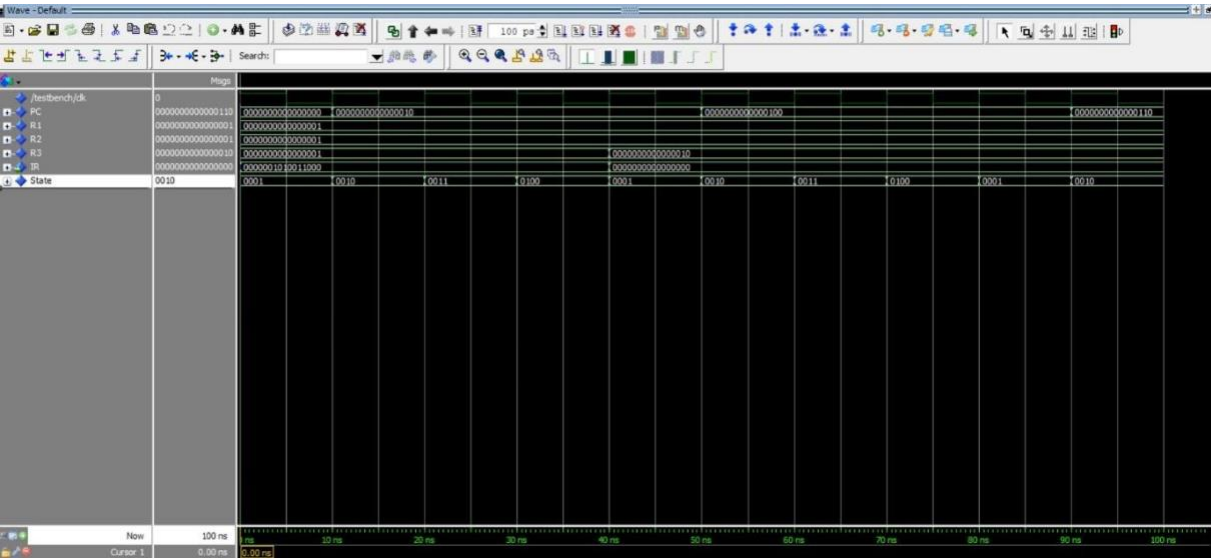


ADI R1 R4 100010

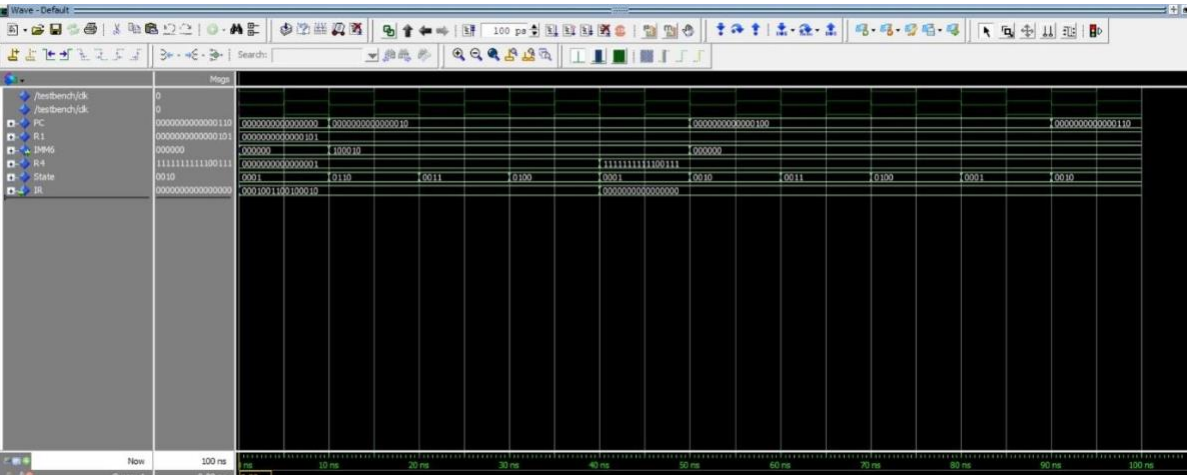


AND R1 R2 R3

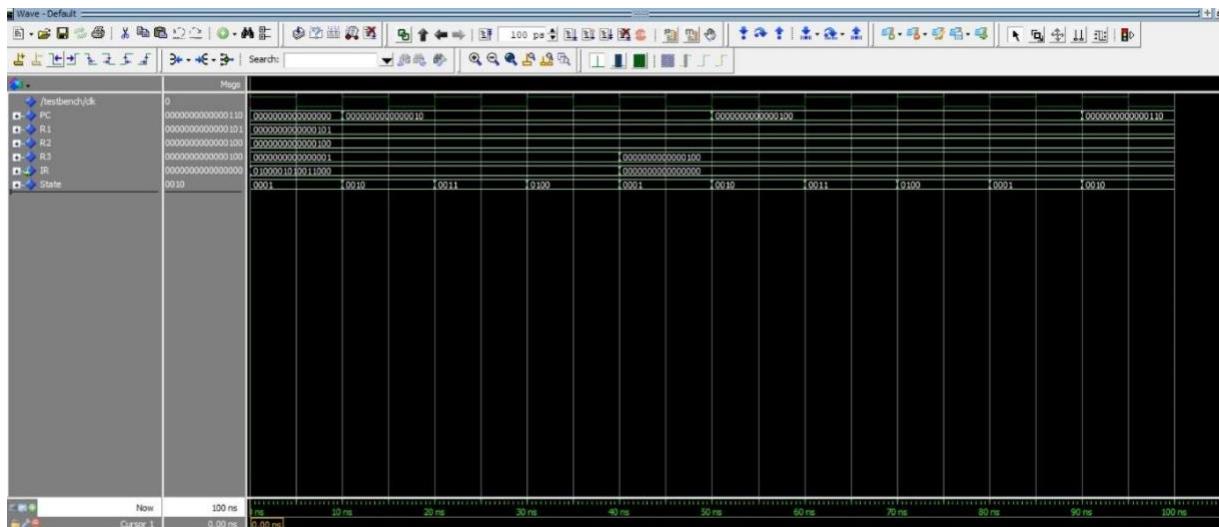


BEQR1 R3000010

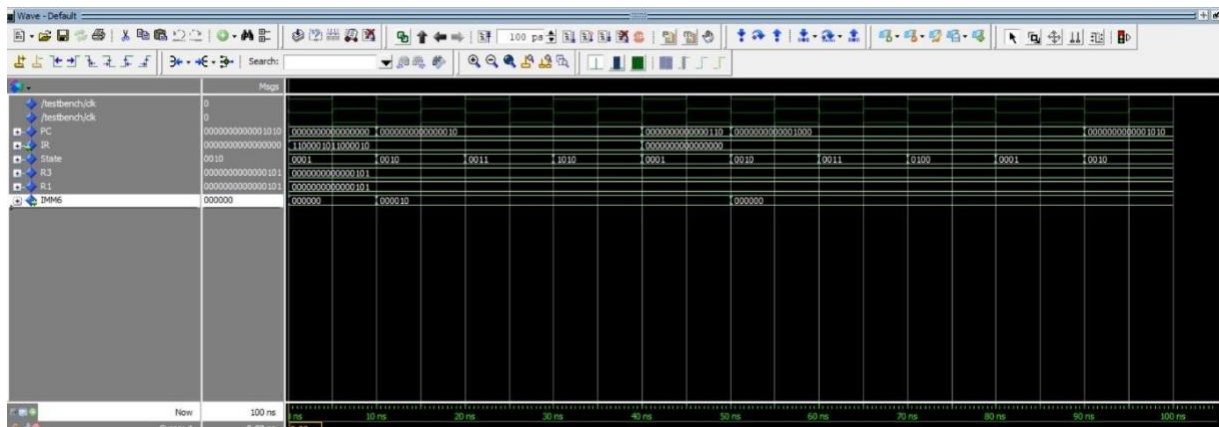


IMP R1 R2 R3

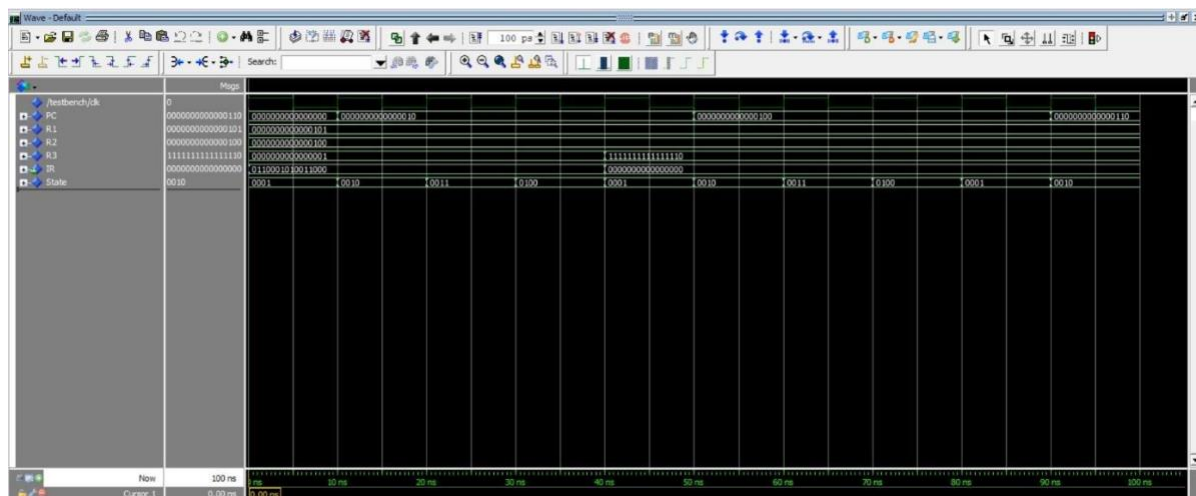


JAL R5 000000011

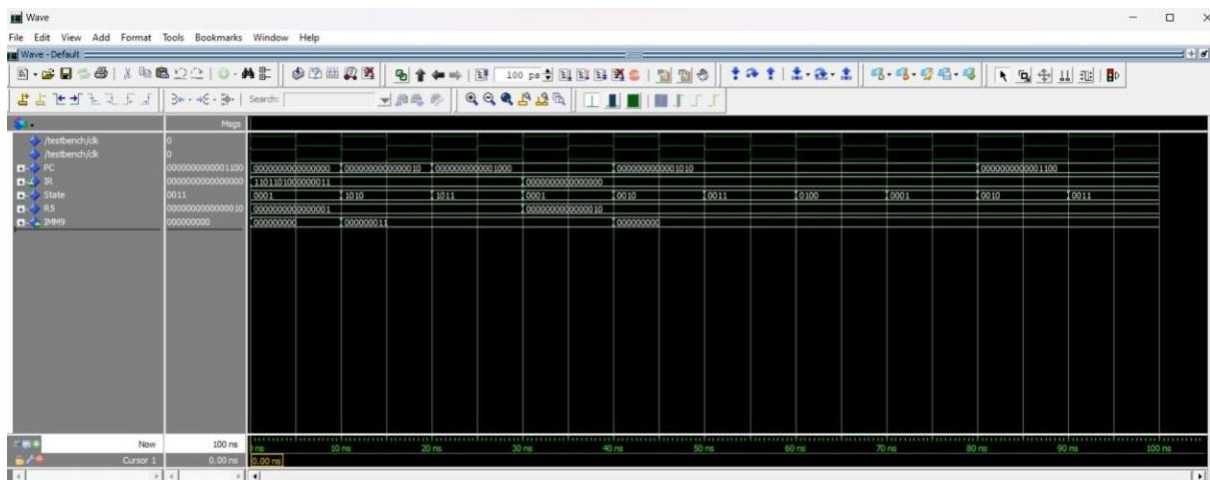

JLR R1 R3 000000

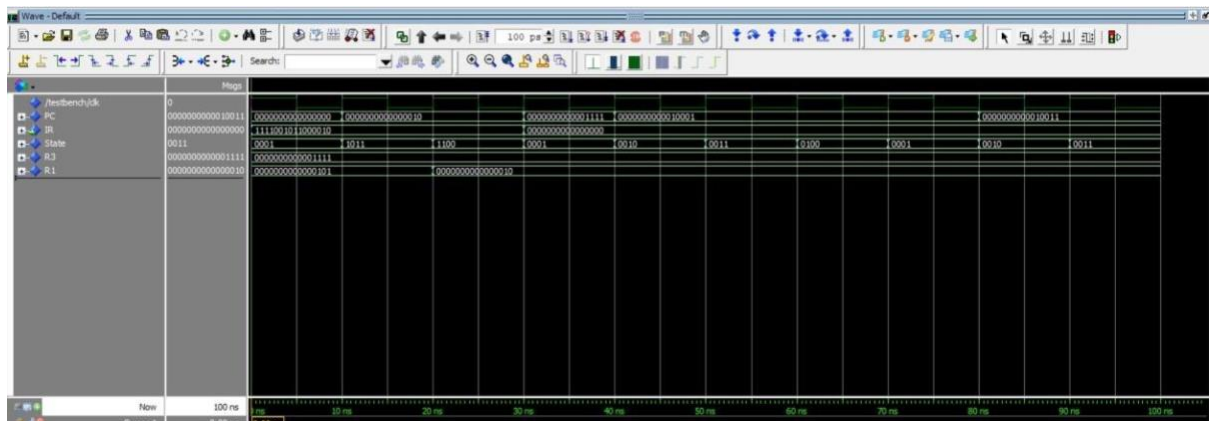


LHI R5 11110101

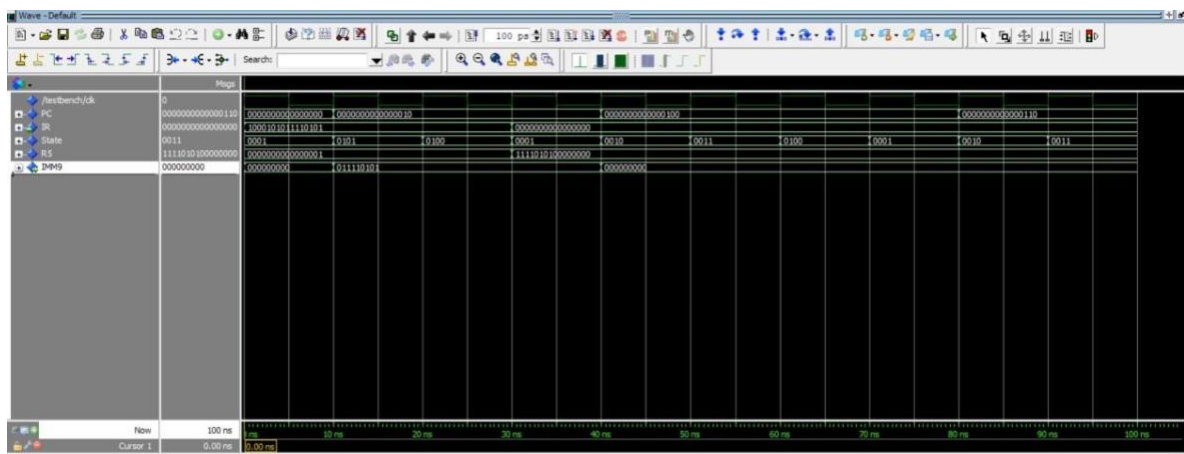


[illegible]

The screenshot shows a digital logic simulation window titled "Wave - Default". The interface includes a top toolbar with various simulation and analysis tools. The main area displays a truth table for a 4-bit adder circuit. The columns are labeled 'A', 'B', 'C', 'D', 'S', 'Cout', 'F', 'G', 'H', 'I', 'J', 'K', 'L', 'M', 'N', 'O', 'P', 'Q', 'R', 'S', 'T', 'U', 'V', 'W', 'X', 'Y', 'Z'. The rows show the binary values of the inputs and outputs for all possible combinations of A, B, C, and D. The bottom status bar shows the current time is 100 ns and the cursor is at 0.00 ns.


SUB R1 R2 R3

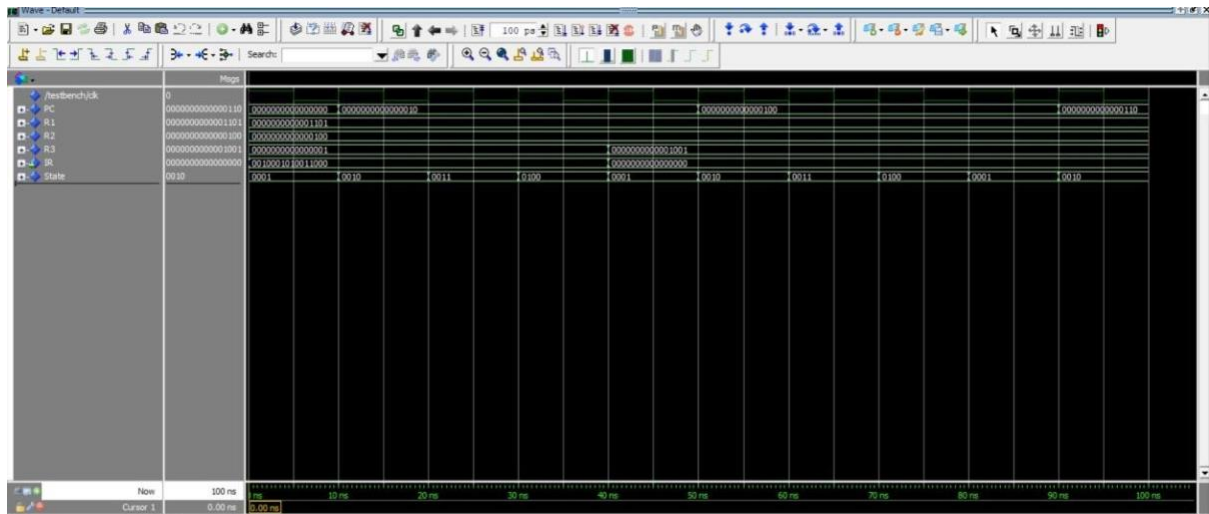

SW R1 R3 000011

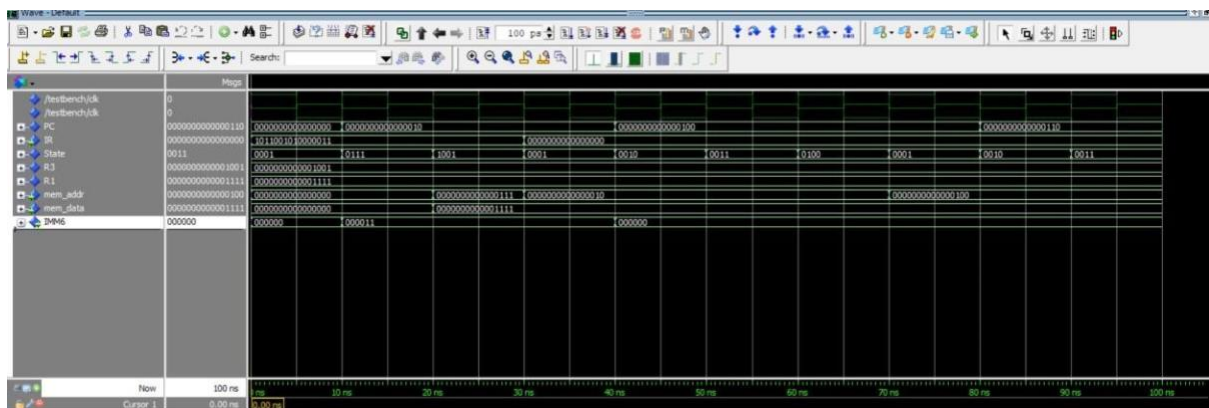

LW R1 R3 000011

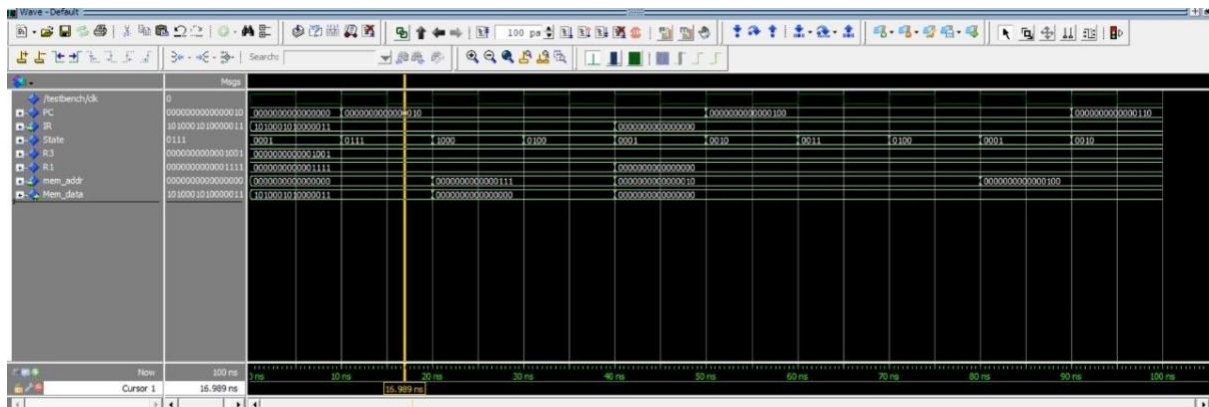

Work Distribution


Aman M - ALU, Registers, Register file, and additional feature. Pin planning for board implementation, added the output signals, tested the board implementation.

Aman R - Initial design of FSM and its VHDL implementation, Shifter, and testing & debugging, created state for reset, solved the issues related to PC. Debugged the latches warning, added the output signals, created a top level entity with outputs for board implementation.

Chinmay - Initial flowcharts of each instruction, Instruction register, SE, Memory, and testing & debugging, final fsm debugged the latches warning. Halt satellite debugging.

Swarup - Initial design of DataPath and its VHDL implementation, Final report and testing & debugging, created state for halt, Combined DataPath And FSM, added the output signals, made changes to memory, final debugging for board implementation with halt.

Complete DataPath

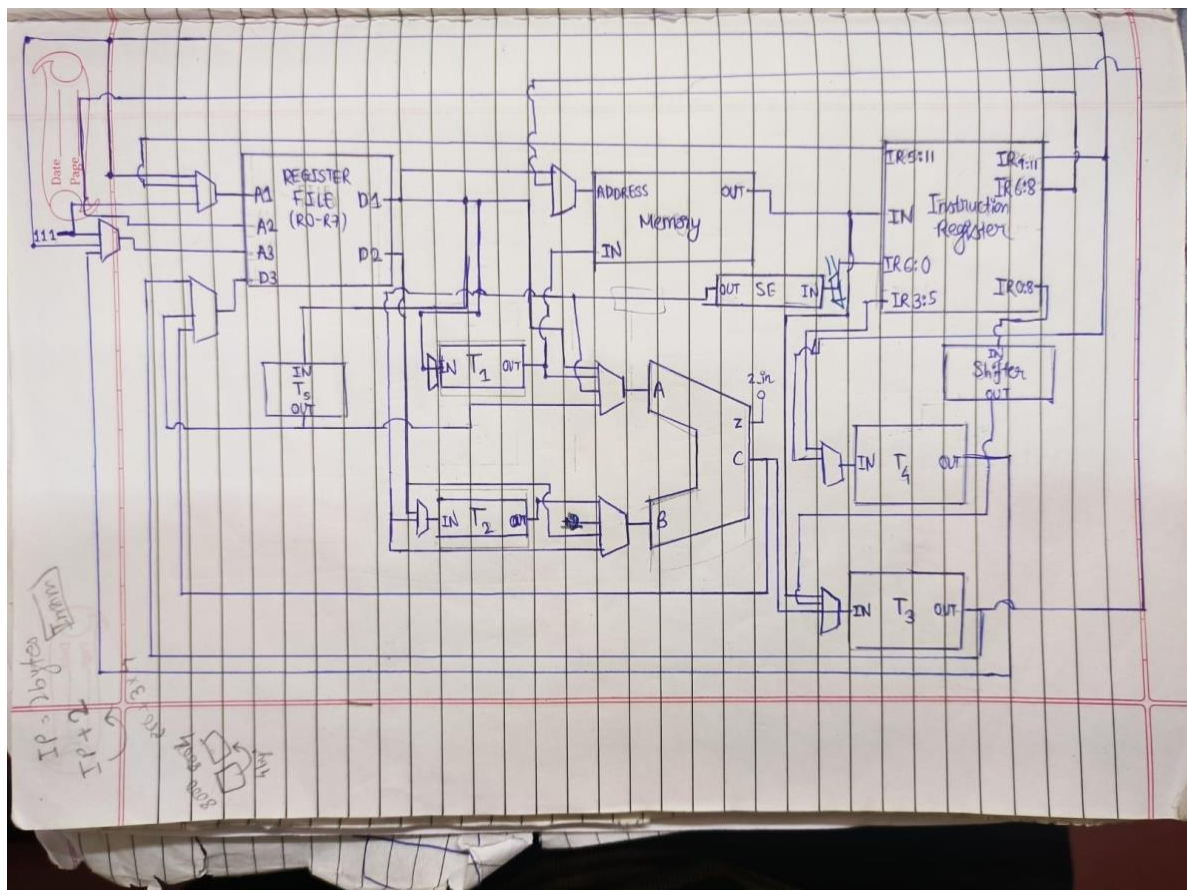

Control Signals

To control the operations of various components in a given state we have used control signals:

- Memory read enable(M_RD)
- Memory write enable(M_WR)
- Instruction register write enable(IR_WR)
- Temporary register1 write enable(T1_WR)
- Temporary register2 write enable(T2_WR)
- Temporary register3 write enable(T3_WR)
- Temporary register4 write enable(T4_WR)
- Temporary register5 write enable(T5_WR)
- Sign extender signals (SE_signal(1) and SE_signal(0))
- Shifter signal (shift_signal(1) and shift_signal(0))
- ALU control signal (ALU_CTRL(2), ALU_CTRL(1) and ALU_CTRL(0))

Most of the signal are like on-off switch but certain control signals depend on the instruction being executed so those signals depend on the opcode.

State	IR_WR	RF_WR	ML_WR	M_RD	T1_WR	T2_WR	T3_WR	T4_WR	T5_WR	Shift_Sg.	SE_Sig	ALU_2	ALU_1	ALU_0
1	1	1	0	1	0	0	0	1	1	x	00	0	0	0
2	0	0	0	0	1	1	0	1	0	x	00	x	x	x
3	0	0	0	0	0	0	1	0	0	x	00	condition 2	condition 1	condition 0
4	0	1	0	0	0	0	0	0	0	x	00	x	x	x
5	0	0	0	0	0	0	1	1	0	op[0]op[1]	00	x	x	x
6	0	0	0	0	1	1	0	1	0	x	01			
7	0	0	0	0	1	0	1	1	0	x	01	0	0	0
8	0	0	0	1	0	0	1	0	0	x	00	x	x	x
9	0	0	1	0	0	0	0	0	0	x	00	x	x	x
10	0	1	0	0	0	0	0	0	0	01	op[0]op[1]	0	0	0
11	0	1	0	0	0	0	0	0	0	x	00	x	x	x
12	0	1	0	0	0	0	0	0	0	x	00	x	x	x

$$\text{condition 0} = !op[0] \cdot (op[1] + op[2])$$

$$\text{condition 1} = op[2] \cdot op[0] + !op[3] \cdot op[2] \cdot !op[1] \cdot !op[0]$$

$$\text{condition 2} = op[2] \cdot (op[0] + op[3])$$

Date _____
Page _____

Significant Changes to Architecture for FPGA Implementation

- **Top-Level Entity:**
 - A new top-level entity named 'Board' has been created. This entity is designed to interface with switches, buttons, and a clock as inputs and outputs through LEDs.
- **Reset Button:**
 - The introduction of a reset button (Button 3) has been implemented. This button is configured to reset the Finite State Machine (FSM), datapath, and other components, except for memory.
- **PC and R7 Handling:**
 - An issue with the Program Counter (PC) and Register 7 (R7) has been addressed. The solution includes the integration of two 2x1 multiplexers to effectively manage the output of R7.
- **Datapath Update:**
 - The datapath has been updated to include the FSM as a component, enhancing the system's modular structure and operational efficiency.
 - Additional output signals such as reg_dp_out and mem_dp_out have been incorporated. These signals store output data and connect with the top-level Board entity for display purposes.
- **FSM State Update:**
 - A new state, termed state 13, has been added to the FSM. This state functions as a reset state, facilitating the storage of data from memory and registers into output signals.
- **Memory Changes:**
 - A significant modification has been made to the memory configuration. The memory has been transitioned from byte addressable to word addressable, aligning with common practices in digital system design.
- **Initialization within Process:**
 - To address warnings related to latches, the design approach was adjusted to initialize signals within the process. This ensures that all signals have defined values, reducing the risk of latch creation, which can lead to unintended behavior in synthesized hardware.
- **FSM and Datapath Integration:**
 - The Finite State Machine (FSM) was merged with the datapath to eliminate unnecessary warnings. This integration streamlined the design, allowing for more efficient communication between the control and data handling segments of the system, and reduced the complexity that could lead to synthesis and implementation issues.
- **Modified FSM**

