



EE-224: Digital Design

IITB-CPU

Instructor: Prof. Virendra Singh

Team ID - 7

Aman Rishal CH – 22b3914

Aman Milind Moon – 22b1216

Chinmay Tripurwar – 22b3902

Swarup Dasharath Patil – 22b3953

Introduction

The IITB-CPU, crafted as a 16-bit computer system, is a foundational architecture designed for educational purposes, particularly for teaching Little Computer Architecture. Featuring eight general-purpose registers (R0 to R7), with Register R7 exclusively assigned to storing the Program Counter (PC), this compact CPU employs a memory addressing scheme where each address corresponds to a single byte. The architecture supports three distinct instruction formats: R, I, and J types, each tailored for specific tasks in executing machine code. In total, the IITB-CPU accommodates 14 instructions, making it a versatile and practical platform for educational exploration.

Major Components Used

1. Memory
The memory is organized as an array with 512 bytes, and each memory location holds 8 bits of data.
2. Register File
The register file consists of eight 16-bit registers of which register R7 is used as a program counter.
3. 5 Temporary registers
The system employs four 16-bit temporary registers and one 3-bit register for quick and versatile data storage during computational tasks.
4. Instruction Register
The Instruction Register, a 16-bit storage unit, holds instructions in the r, i, or j format
5. ALU
The ALU (Arithmetic Logic Unit) performs operations like addition, subtraction, multiplication, logical OR, logical AND, and implication on two 16-bit numbers within the computer system.
6. Sign Extender
The sign extender extends either a 6-bit or 9-bit number to a 16-bit number based on the control signal, preserving the sign bit for accurate representation in the computer system.
7. Shifter
The shifter performs either left shifts or right shifts on binary data, governed by the control signal, within the computer system.

States

Description:

State 1: Read from memory and increment PC

State 2: Read Instruction (R Type)

State 3: Execute Specific ALU operation

State 4: Update Result

State 5: Read Instruction (LHI/LLI)

State 6: Read Instruction (ADI)

State 7: Read Instruction (LW/SW)

State 8: Read from memory

State 9: Write to memory

State 10: Branch to PC + Imm*2

State 11: PC to Reg. A


State 12: Branch to Reg. B

State Flowcharts

States	Data Transfer	Control Signal
S1	111 → RF_A1 RF_D1 → MEM_ADD MEM_OUT → IR RF_D1 → ALU_A +2 → ALU_B ALU_C → RF_D3 111 → RF_A3 RF_D1 → T5	M_RD IR_W ALU_CTRL RF_WR T5_WR
S2	IR_11_9 → RF_A1 IR_8_6 → RF_A2 RF_D1 → T1 RF_D2 → T2 IR_5_3 → T4	T1_WR T2_WR T4_WR
S3	T1 → ALU_A	ALU_CTRL


	T2 → ALU_B ALU_C → T3 ALU_Z → Zin	T3_WR
S4	T3 → RF_D3 T4 → RF_A3	RF_WR
S5	IR_8_0 → SHIFTER_IN SHIFTER_OUT → T3 IR_11_9 → T4	SHIFT_SIGNAL T3_WR T4_WR
S6	IR_11_9 → RF_A1 RF_D1 → T1 IR_8_6 → T4 IR_5_0 → SE_IN_6 SE_OUT → T2	T1_WR T2_WR SE_SIGNAL T4_WR
S7	IR_11_9 → T4 IR_5_0 → SE_IN_6 SE_OUT → ALU_A IR_8_6 → RF_A2 RF_D2 → ALU_B ALU_C → T3 IR_11_9 → RF_A1 RF_D1 → T1	T4_WR SE_SIGNAL ALU_CTRL T3_WR T1_WR
S8	T3 → MEM_ADD MEM_OUT → T3	M_RD
S9	T1 → MEM_IN T3 → MEM_ADD	M_WR
S10	T5 → ALU_A IR_5_0 → SE_IN_6 IR_8_0 → SE_IN_9 SE_OUT → SHIFTER_IN SHIFTER_OUT → ALU_B ALU_C → RF_D3 111 → RF_A3	SE_SIGNAL SHIFTER_SIGNAL ALU_CTRL RF_WR
S11	TR_11_9 → RF_A3 T5 → RF_D3	RF_WR
S12	IR_8_6 → RF_A2 RF_D2 → RF_D3 111 → RF_A3	RF_WR

FSM

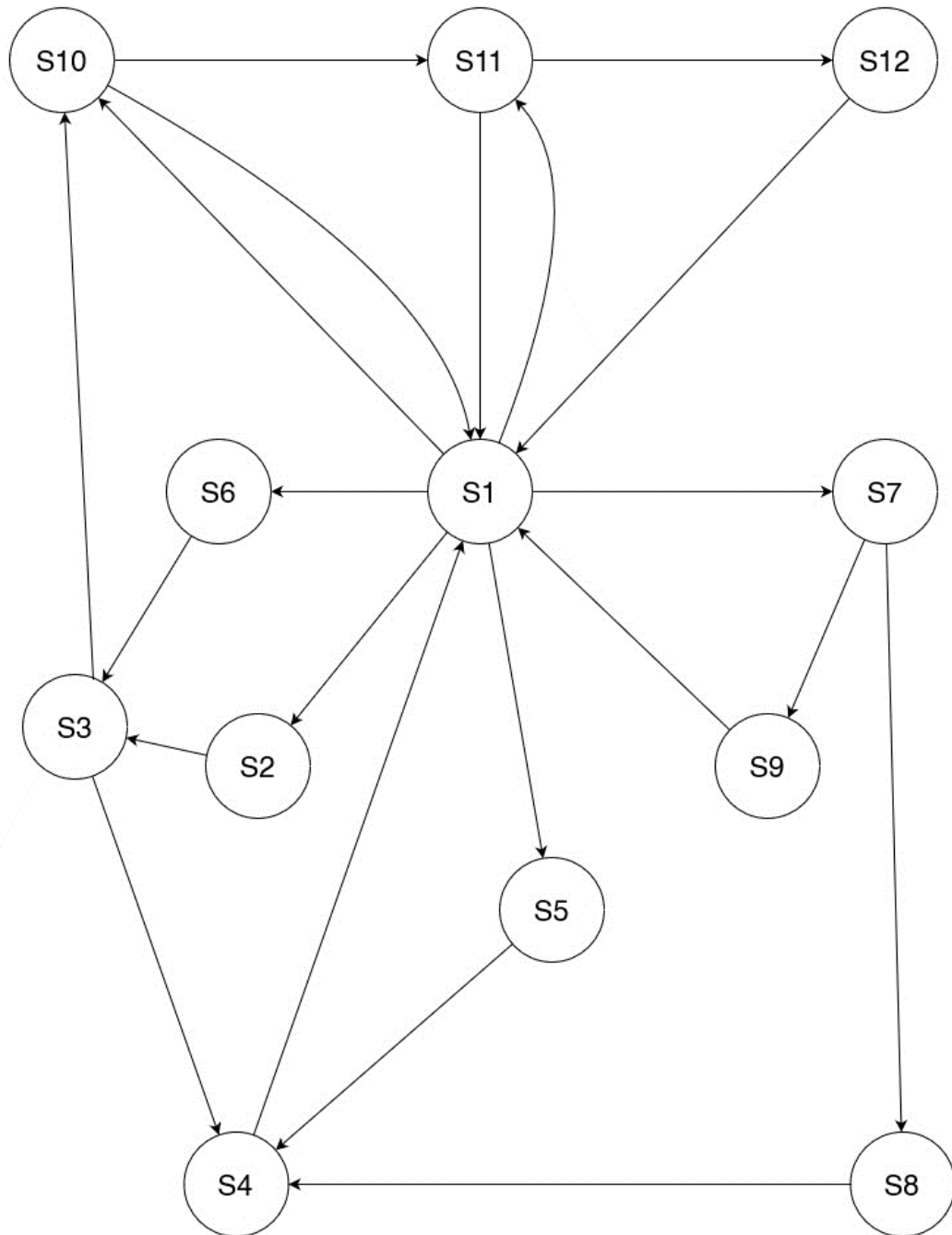


STATE FLOW DIAGRAM


ALU

 


J- Type

 


ADI

 


LW

 


SW

 


BEQ

 

JAL

 


JLR

 


RTL SIMULATIONS


ADD R1 R2 R3

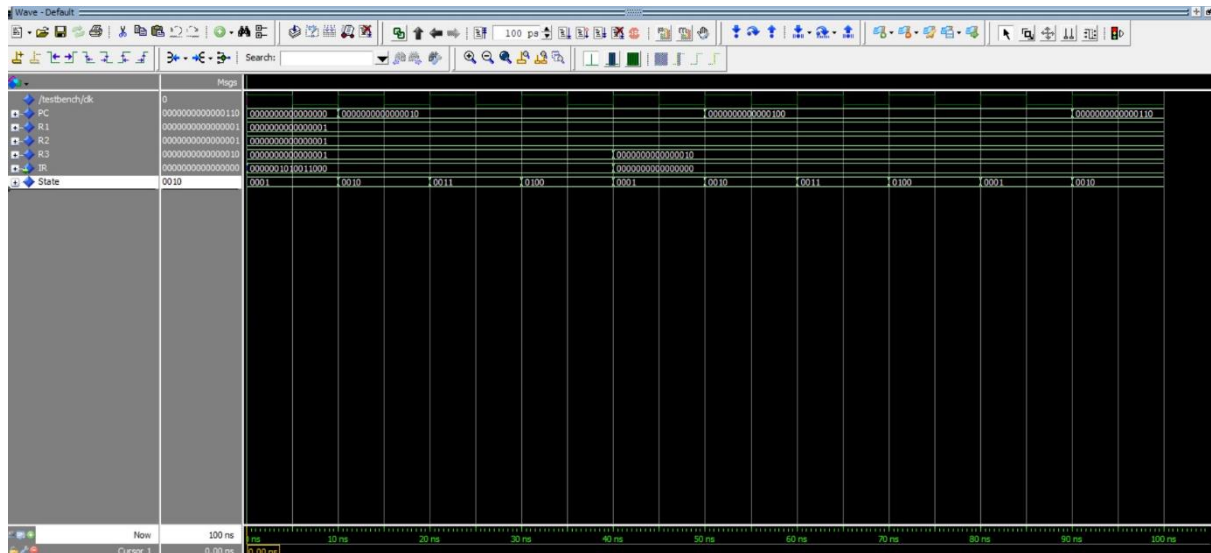


ADI R1 R4 100010

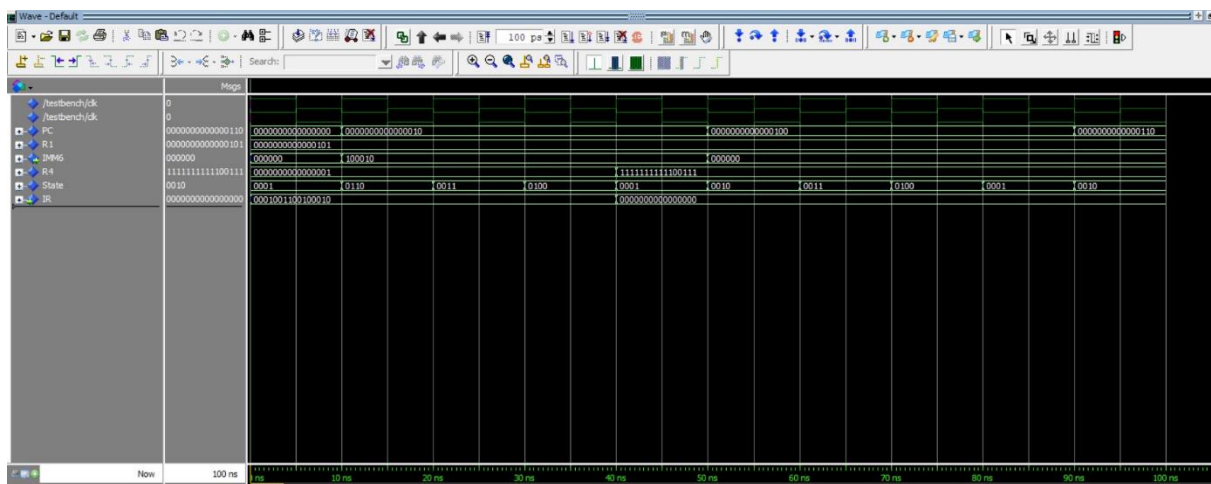


AND R1 R2 R3

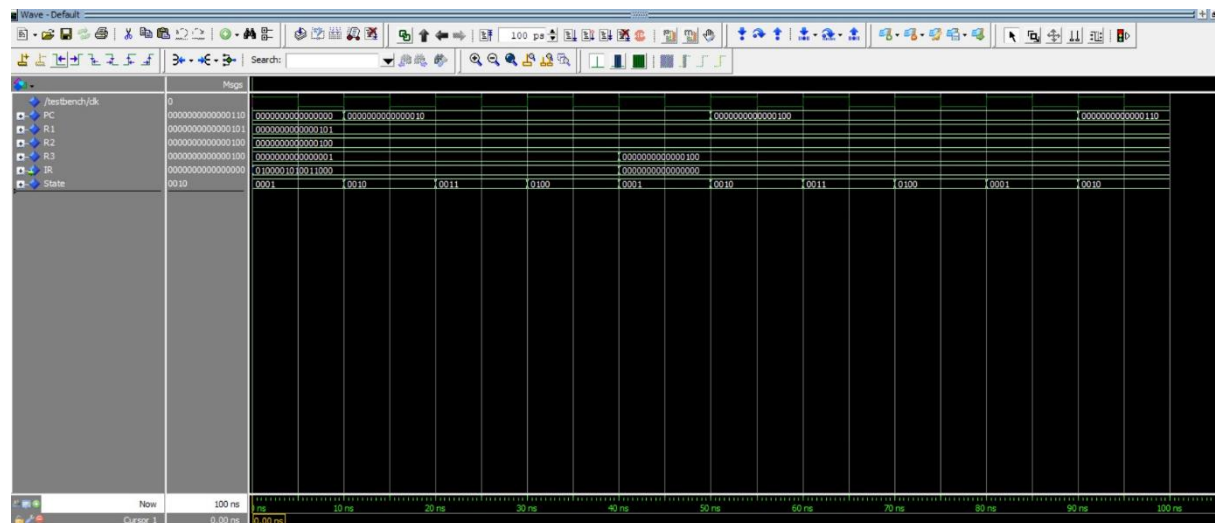


BEQR1 R3000010

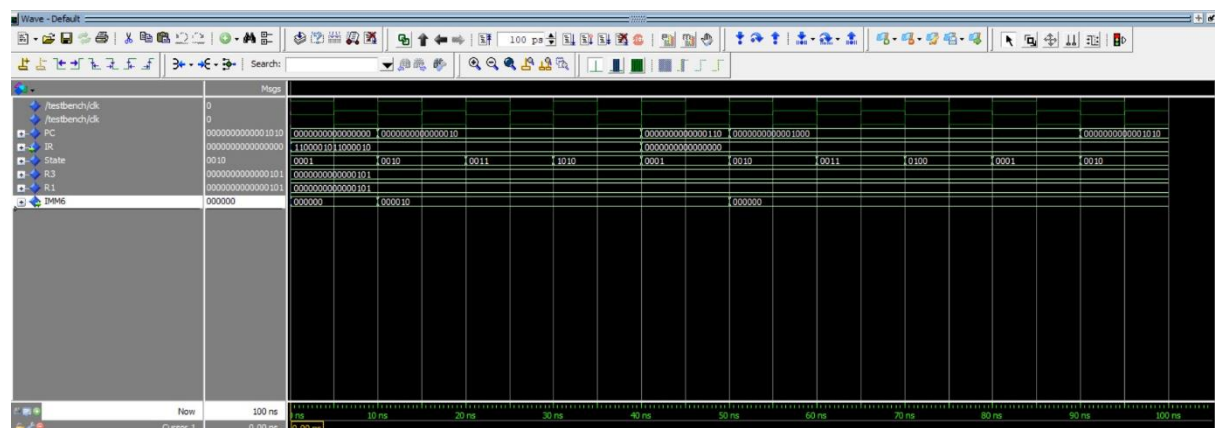


IMP R1 R2 R3

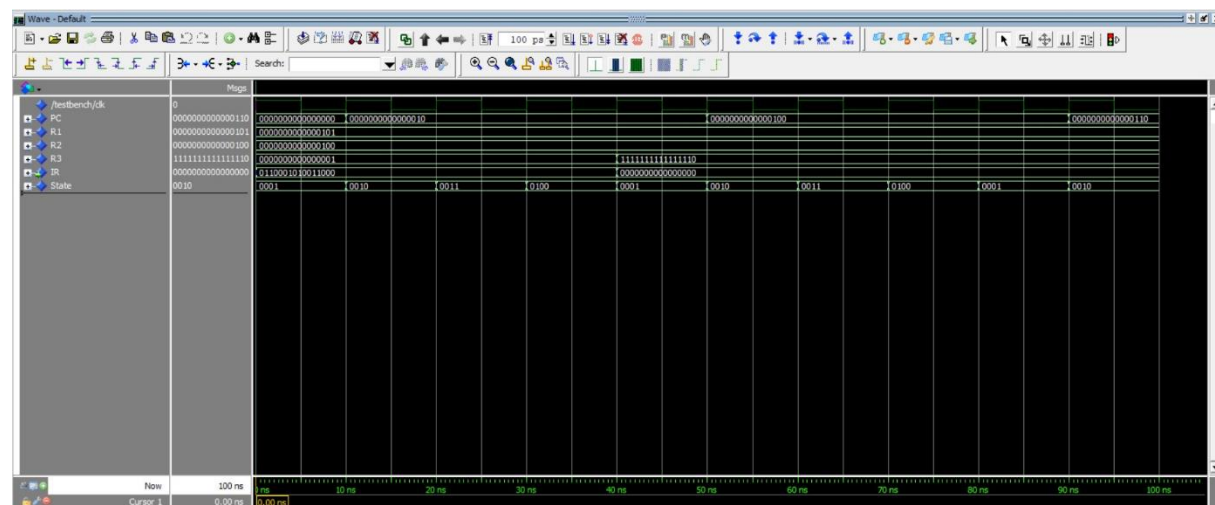


JAL R5 000000011

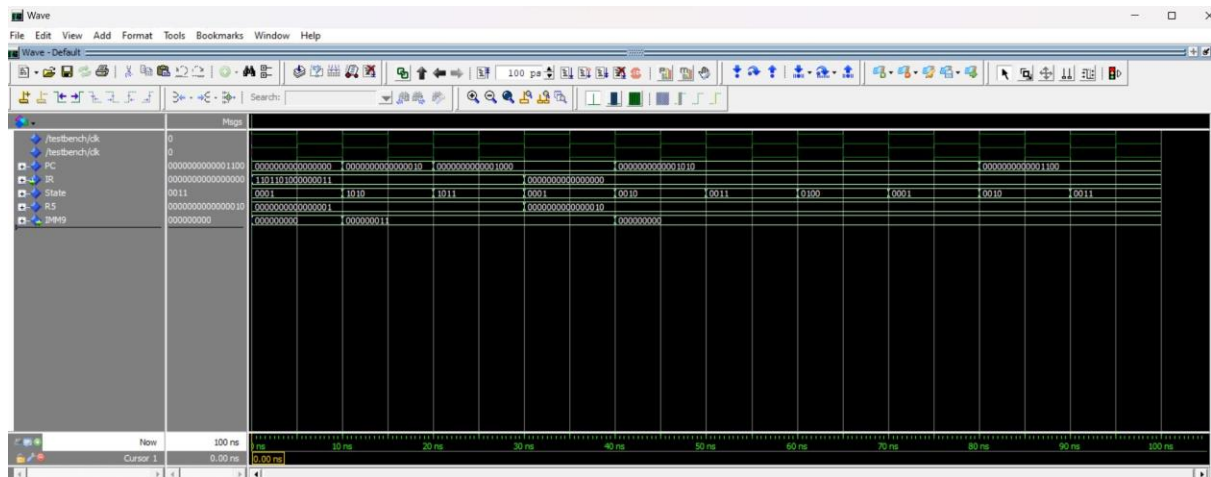


JLR R1 R3 000000

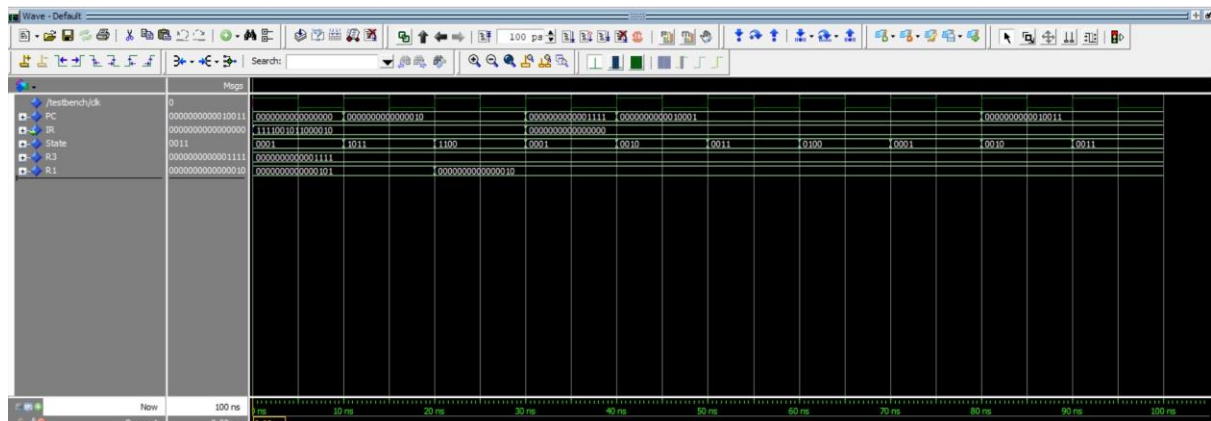


LHI R5 11110101

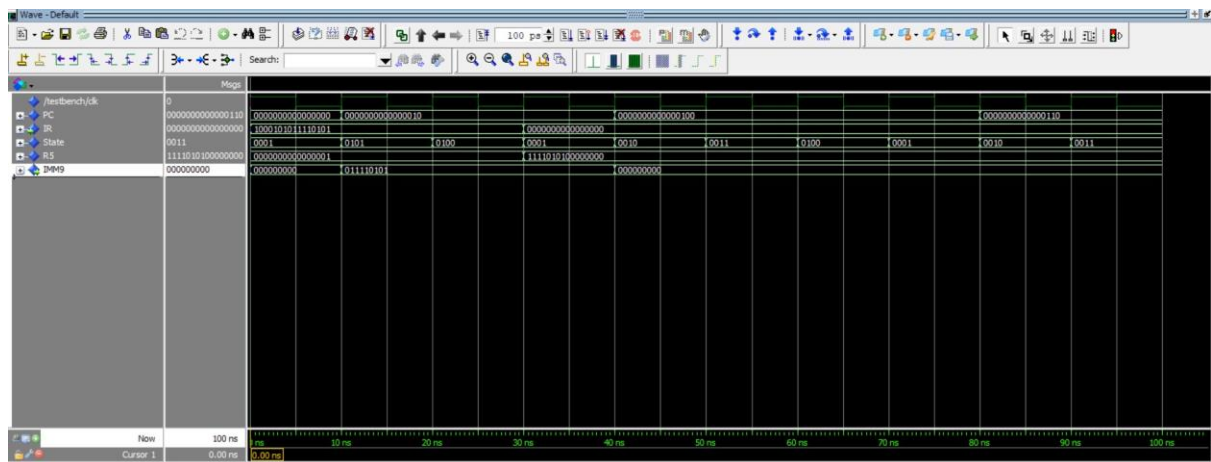


LLI R5 11110101

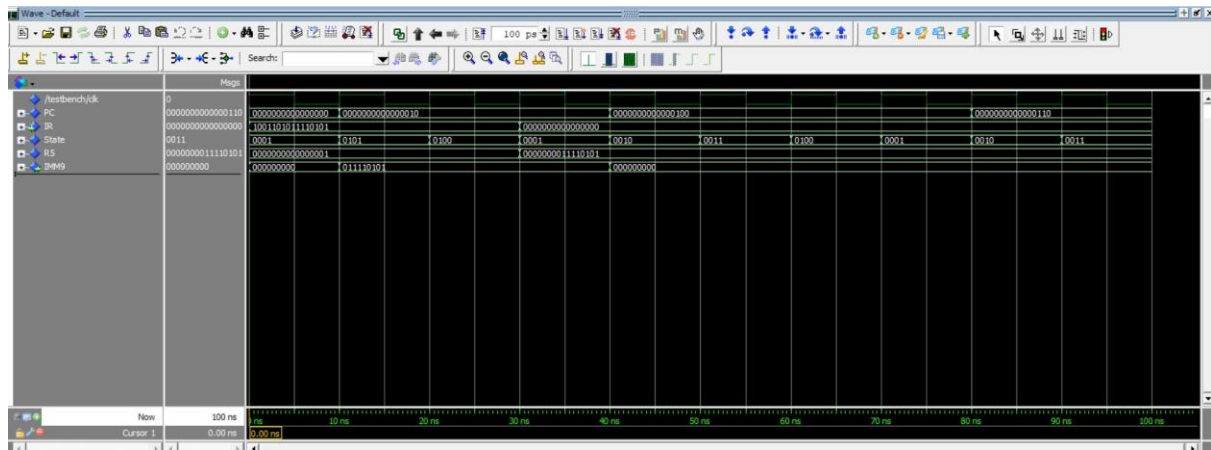


MUL R1 R2 R3

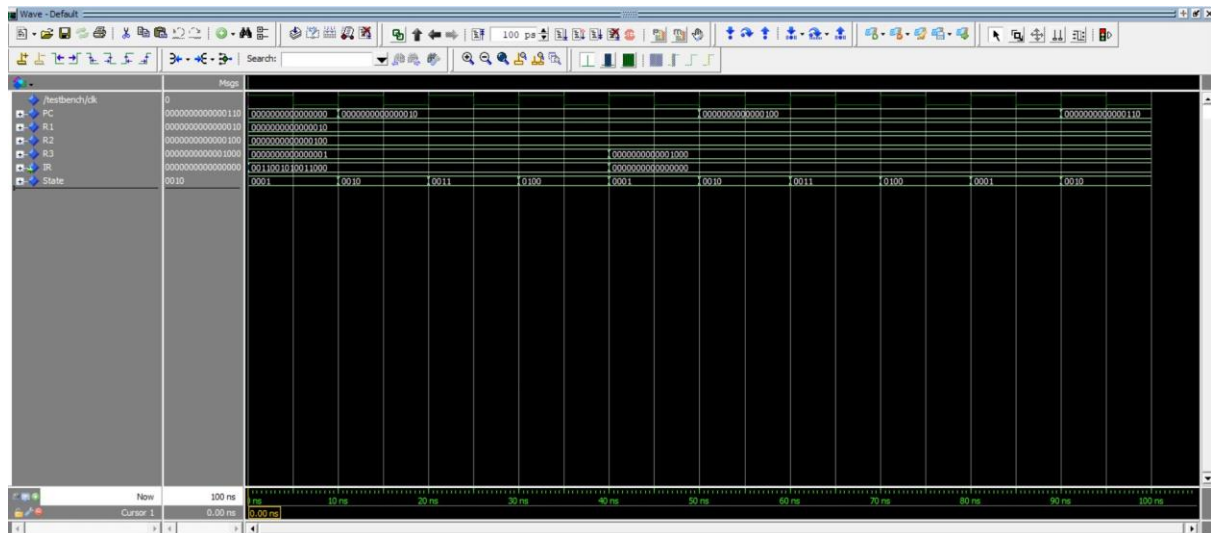


ORA R1 R2 R3

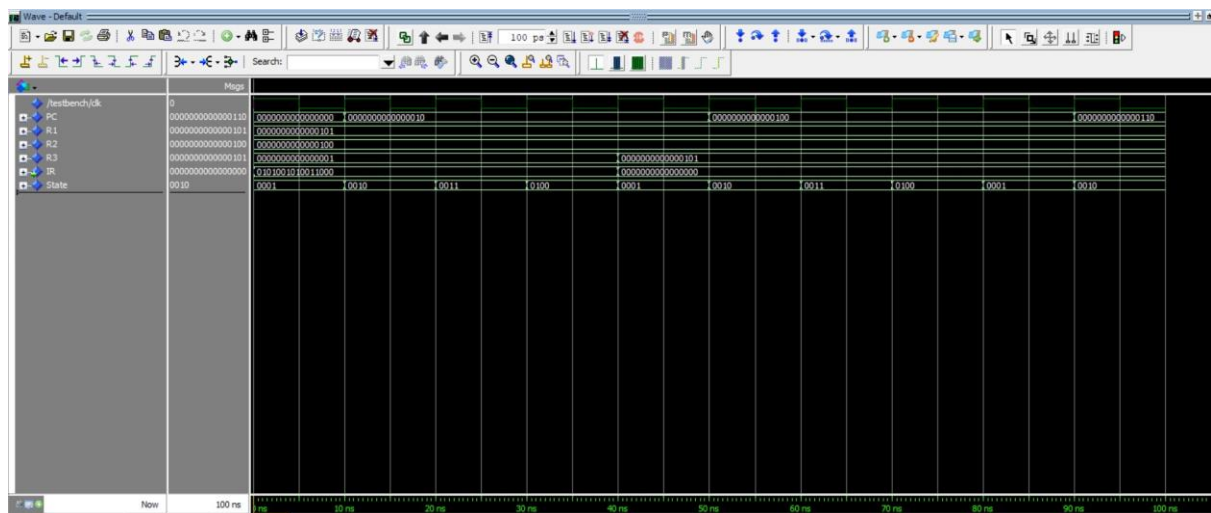


SUB R1 R2 R3

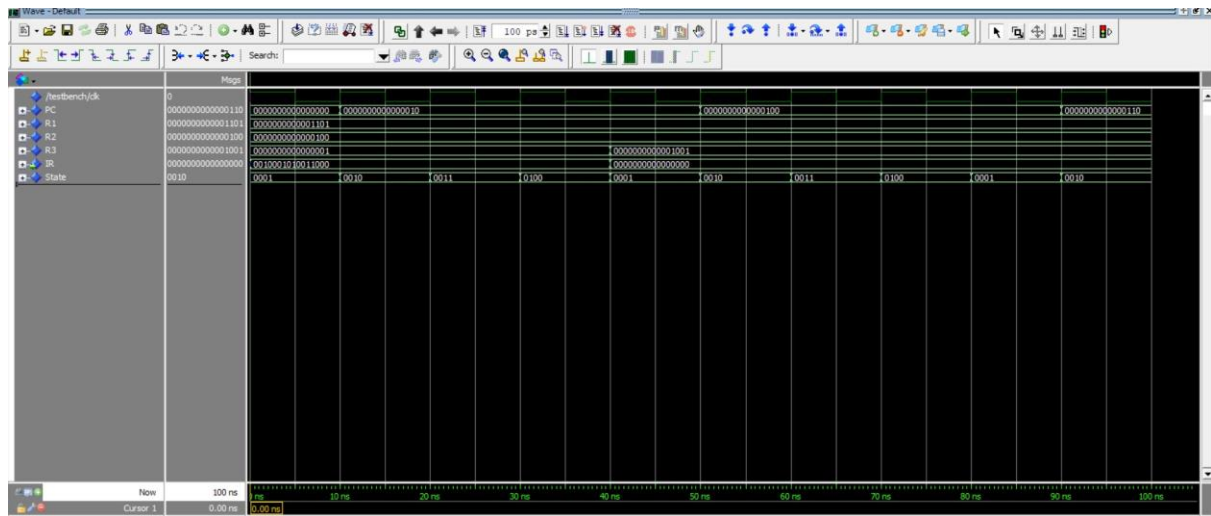

SW R1 R3 000011

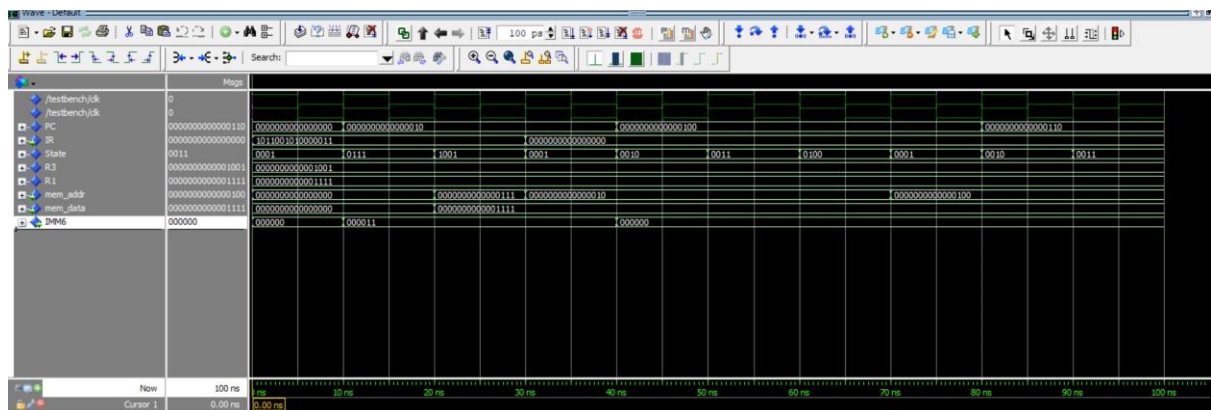

LW R1 R3 000011

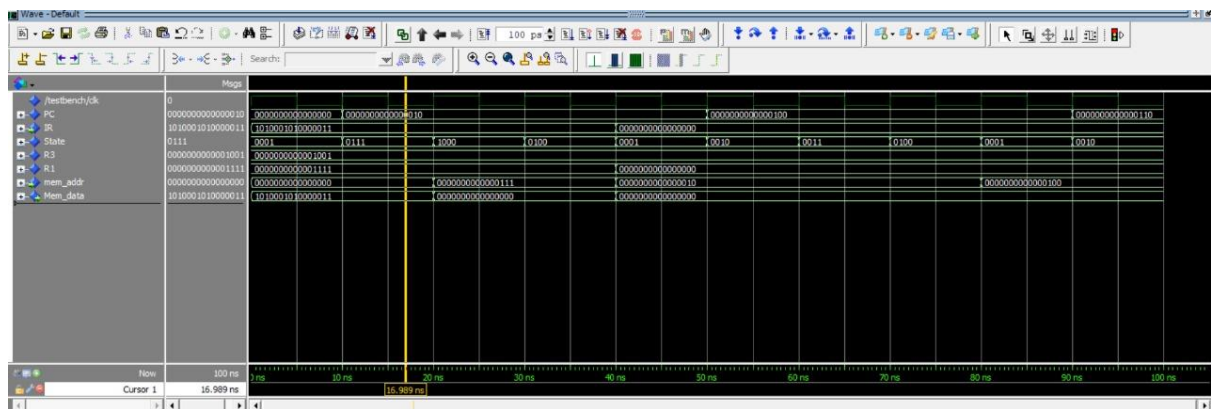

Work Distribution


Aman M - ALU , Registers , Register file and additional feature.

Aman R - Initial design of FSM and its VHDL implementation , Shifter and testing & debugging

Chinmay - Initial flowcharts of each instruction, Instruction register, SE , Memory and testing & debugging

Swarup - Initial design of DataPath and its VHDL implementation ,Final report and testing & debugging

Complete DataPath

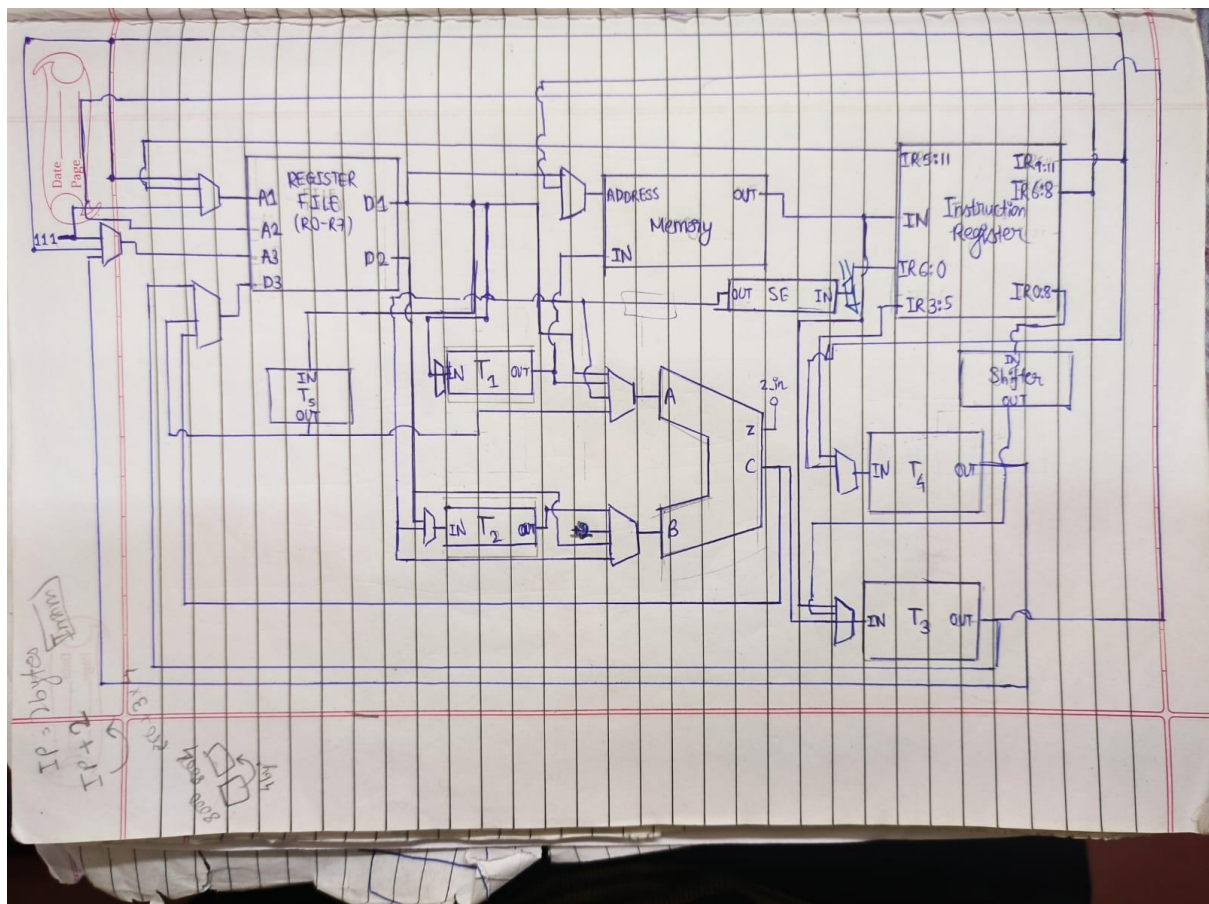

Control Signals

In order to control the operations of various components in a given state we have used control signals:

- Memory read enable(M_RD)
- Memory write enable(M_WR)
- Instruction register write enable(IR_WR)
- Temporary register1 write enable(T1_WR)
- Temporary register2 write enable(T2_WR)
- Temporary register3 write enable(T3_WR)
- Temporary register4 write enable(T4_WR)
- Temporary register5 write enable(T5_WR)
- Sign extender signals (SE_signal(1) and SE_signal(0))
- Shifter signal (shift_signal(1) and shift_signal(0))
- ALU control signal (ALU_CTRL(2), ALU_CTRL(1) and ALU_CTRL(0))

Most of the signal are like on-off switch but certain control signals depend on the instruction being executed so those signals depend on the opcode.

State	IR_WR	RE_WR	MLWR	M_RD	T1_WR	T2_WR	T3_WR	T4_WR	T5_WR	Shift_Sg.	SE_Sig	ALU_2	ALU_1	ALU_0
1	1	1	0	1	0	0	0	1	x	00	00	0	0	0
2	0	0	0	0	1	1	0	1	0	x	00	x	x	x
3	0	0	0	0	0	0	1	0	0	x	00	condition2	condition1	condition0
4	0	1	0	0	0	0	0	0	0	x	00	x	x	x
5	0	0	0	0	0	0	1	1	0	op[0]op[1]	00	x	x	x
6	0	0	0	0	1	1	0	1	0	x	01	0	0	0
7	0	0	0	0	1	0	1	0	0	x	01	0	0	0
8	0	0	0	1	0	0	1	0	0	x	00	x	x	x
9	0	0	1	0	0	0	0	0	0	x	00	x	x	x
10	0	1	0	0	0	0	0	0	0	01	op[0]op[1]	0	0	0
11	0	1	0	0	0	0	0	0	0	x	00	x	x	x
12	0	1	0	0	0	0	0	0	0	x	00	x	x	x

$$\text{condition 0} = !op[0] \cdot (op[1] + op[2])$$

$$\text{condition 1} = op[3] \cdot op[0] + !op[3] \cdot op[2] \cdot !op[1] \cdot !op[0]$$

$$\text{condition 2} = op[2] \cdot (op[0] + op[3])$$

Date _____
Page _____